

Component Design Approach and Layout Consideration of G-NAVP™ Topology

Abstract

In the design procedure, the component design and PCB layout greatly affect the performance of power supply. Careful PCB layout is critical to achieve low switching losses and clean, stable operation. Choosing appropriate component make the power supply easy passing the specifications of Intel and AMD. This application note will introduce the design approach of G-NAVP™ control topology, including on-time setting, switching frequency setting, load-line setting, and DCR current sensing network setting. After that, the recommend PCB layout rules will be showed to avoid noise interference to make the controller more robust.

1. Design Approach and Component Selection

The following design approach will use RT8884B as an example, which is designed to meet Intel VR12.5 specification. There are three main design procedures for RT8884B. The first step is initial settings for on-time and switching frequency. The second step is the DCR current sensing network design. Finally, we have to complete the load line design.

CPU Operation Condition	
Input Voltage	12V
No. of Phases	3
V _{BOOT}	1.7V
V _{DAC(MAX)}	1.85V
I _{CCMAX}	106A
I _{CC-DY}	60A
I _{CC-TDC}	55A
Load Line	1.5mΩ
Fast Slew Rate	12.5mΩ/μs
Max Switching Frequency	300kHz

Refer to Shark Bay VRTB power delivery guide, the recommended output filter is listed as follows :

Output Inductor : 360nH / 0.72mΩ

Output Bulk Capacitor : 560μF / 2.5V / 5mΩ (max) 4 to 5pcs

Output Ceramic Capacitor : 22μF / 0805 (18pcs max sites on top side)

1.1. Initial Setting for On-Time and Switching Frequency

Generally, higher switching frequency can achieve faster transient response, smaller steady-state output ripple, and reduce power components' size and PCB space. However, the higher switching frequency will cause lower conversion efficiency, poor noise immunity and thermal issue. Therefore, the maximum switching frequency needs to be limited in a reasonable range to compromise between the pros and cons. After determining the maximum switching frequency, the maximum on-time can be obtained with the relation between the duty and switching frequency.

$$t_{on(MAX)} = \frac{1}{f_{sw,max}} \cdot \frac{V_{DAC(MAX)}}{V_{IN(MAX)}} \quad (1)$$

Where V_{DAC} is the reference voltage, $f_{sw,max}$ is the maximum switching, and $V_{IN(MAX)}$ is the maximum input voltage. The following shows the design example of RT8884B.

$$t_{on(MAX)} = \frac{1}{300k} \cdot \frac{1.85}{12} = 514 \text{ (ns)}$$

Since RT8884B is one kind of constant on-time control, the patented CCRCOT (Constant Current Ripple COT) technology can generate an adaptive on-time with input voltage and VID code to obtain a constant current ripple. So that the output voltage ripple can be controlled nearly like a constant at different input and output voltage operation range. Connect a resistor R_{TON} between input voltage terminal and TONSET pin to set the on-time width.

$$t_{on} = \frac{R_{ton} \cdot C \cdot 2.2}{V_{IN} - V_{DAC}} \quad (V_{DAC} < 2.2V)$$

$$t_{on} = \frac{R_{ton} \cdot C \cdot V_{DAC}}{V_{IN} - V_{DAC}} \quad (V_{DAC} \geq 2.2V) \quad (2)$$

where $C = 18.2pF$

Where V_{IN} is the maximum input voltage, V_{DAC} is the reference voltage, and t_{on} is the on-time which is determined in the above equation. The following shows the design example of RT8884B.

$$514n = \frac{R_{ton} \cdot 18.2p \cdot 2.2}{12 - 1.85} \Rightarrow R_{ton} = 130k\Omega$$

1.2. DCR Current Sensing Network Design

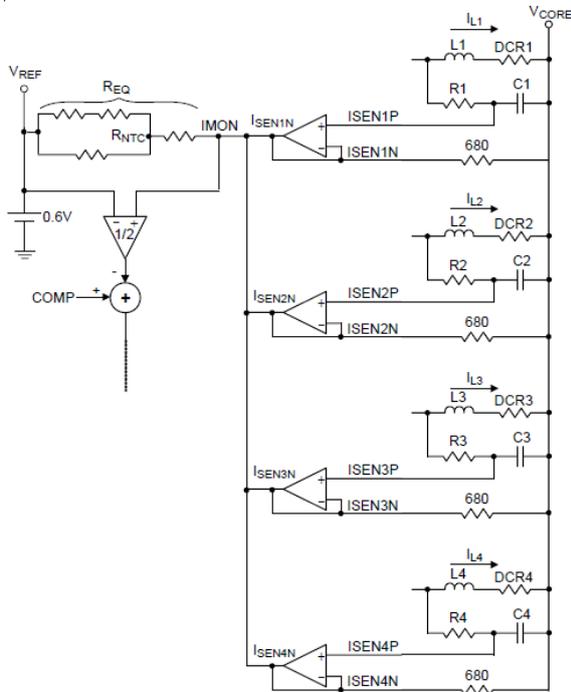


Figure 1. The whole current loop structure of RT8884B.

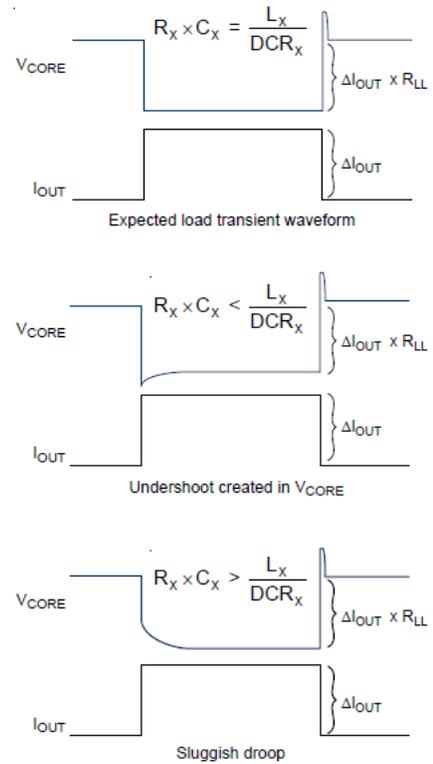


Figure 2. The corresponding output waveforms with different τ_{Cx} and τ_{Lx} time constant.

Figure 1 shows the whole current loop structure of RT8884B. The design of DCR current sensing network plays an important role in both ACLL performance and DCLL accuracy. For different time constant design, the ACLL behavior can be separated into three conditions as follows. Moreover, Figure 2 shows the corresponding output waveforms with different τ_{Cx} and τ_{Lx} time constant.

- If τ_{Cx} matches τ_{Lx} , an expected load transient waveform can be designed.
- If τ_{Cx} is larger than τ_{Lx} , output voltage has a sluggish droop as load increasing.
- If τ_{Cx} is smaller than τ_{Lx} , output voltage will sag to reduce the margin of undershoot specification.

$$\begin{aligned} \tau_{Cx} &= R_x \cdot C_x \\ \tau_{Lx} &= \frac{L_x}{DCR_x} \end{aligned} \tag{3}$$

Where DCR_x is the equivalent resistance of the inductor, L_x is the inductance of the inductor, and R_x and C_x is the DCR current sensing network parameters.

Usually, the τ_{Cx} time constant will be designed equal or slightly larger than the τ_{Lx} time constant to prevent the overshoot and undershoot to have more margin to pass the specification. Notice that, the C_x may attenuate because of the bias voltage, temperature, or frequency...etc. As design the DCR current sensing network, the attenuate effect on the C_x is needed to be considered.

Since the copper wire of inductor has a positive temperature coefficient, DCR value is increased linearly with an increase of load current. Therefore, for achieving a better DCLL performance, a thermal compensation network with NTC thermister (R_{EQ}) is necessary to compensate the positive temperature coefficient of inductor DCR. The detailed thermal compensation can refer to design tool for specific product.

1.3. Load-Line Design

In the G-NAVP™ topology, the load line design depends on the ratio of current loop gain and voltage loop gain. The detailed load line equation will be shown in the corresponding IC datasheet. The following is using RT8884B as an example.

$$R_{LL} = \frac{A_I}{A_V} = \frac{\frac{1}{2} \cdot \frac{DCR}{R_{CS}} \cdot R_{EQ}}{\frac{R_2}{R_1}} \quad (\text{m}\Omega) \quad (4)$$

Where $DCR (25^\circ\text{C}) = 0.72\text{m}\Omega$, $R_{CS} = 680\Omega$ is the current sensing resistor, $R_{EQ} (25^\circ\text{C})$ is designed for the thermal compensation, and the R_2 / R_1 is the compensator A_V gain. Through this equation, the load line can be changed simply by adjusting the compensator A_V gain. Following Intel VR12.5 specification, a $1.5 (\text{m}\Omega)$ load line is required; therefore, the R_2 / R_1 A_V gain can be decided. The design example of RT8884B is shown as below.

$$\frac{R_2}{10\text{k}} = \frac{\frac{1}{2} \cdot \frac{DCR}{R_{CS}} \cdot R_{EQ}}{R_{LL}} = \frac{\frac{1}{2} \cdot \frac{0.72\text{m}}{680} \cdot 16.8\text{k}}{1.5\text{m}} \Rightarrow R_2 = 59.2\text{k}$$

2. Layout Consideration

Careful PC board layout is critical to achieve low switching losses and clean, stable operation. The switching power stage requires particular attention. If possible, mount all of the power components on the top side of the board with their ground terminals flushed against one another. Follow these guidelines for optimum PC board layout :

2.1. Power Stage Layout Guideline

- Keep the high current paths short, especially at the ground terminals.
- Keep the power traces and load connections short. This is essential for high efficiency.
- When trade-off between the charging path and the discharging path of the inductor, it's preferable to let the inductor charging path longer than the discharging path.

2.2. IC Sensing Pad and RGND Layout Guideline

- Place the current sense component (C_x , R_{CSx} , R_x) close to the controller to avoid the current sensing signals be coupled by the noise.

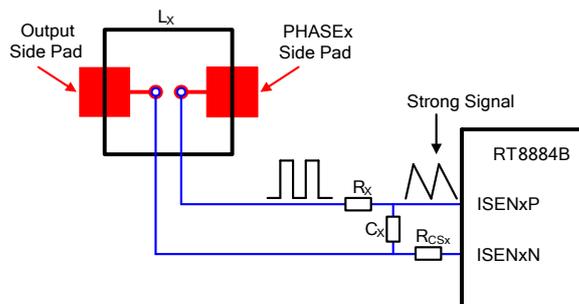


Figure 3. Placement of current sensing components.

- ISENxP and ISENxN connections for current limit and voltage positioning must be made using Kelvin sense connections to guarantee current sense accuracy. The traces from the inductor are run directly from the inductor pad and not from the connection plane of the inductor.

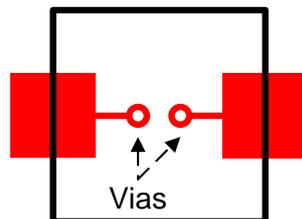


Figure 4. The inductor pad for current sensing traces.

- The PCB trace from the inductor sense nodes should be paralleled back to the controller. Typically these traces are run underneath the inductors on the bottom layer of PCB. If these traces run on an inner layer, there must be a ground plane above the current sense traces as a shielding from the top layer.
- Route high speed switching nodes (PWM, UG, LG, phase, etc...) away from sensitive analog areas (COMP, FB, ISENxP, ISENxN, etc...).
- Users need to connect exposed pad to the ground plane through low impedance path. The use of at least 5 vias to connect to ground planes in PCB internal layers is recommended.

3. Experimental Result and Conclusion

3.1. Experimental Result

Figure 5 shows the RT8884B EVB sample, which is applied in VR12.5 applications and can support 4/3/2/1 phase. The measured load line curve and efficiency is shown in Figure 6. From the measured result, the G-NAVP™ topology can provide an accurate load line and still maintain the higher efficiency. Figure 7 shows a large step and a small step load transient waveform, which indicates fast and stable transient performance and proper AVP control.



Figure 5. The EVB sample of RT8884B.

Table 1. EVB testing condition

V _{IN}	12V
V _{OUT}	1.8V @PS0
Phase Number	4
LS	360nH / 0.72mΩ
Co	OSCON : 470μF / 4.5mΩ*4 MLCC : 22μF*19


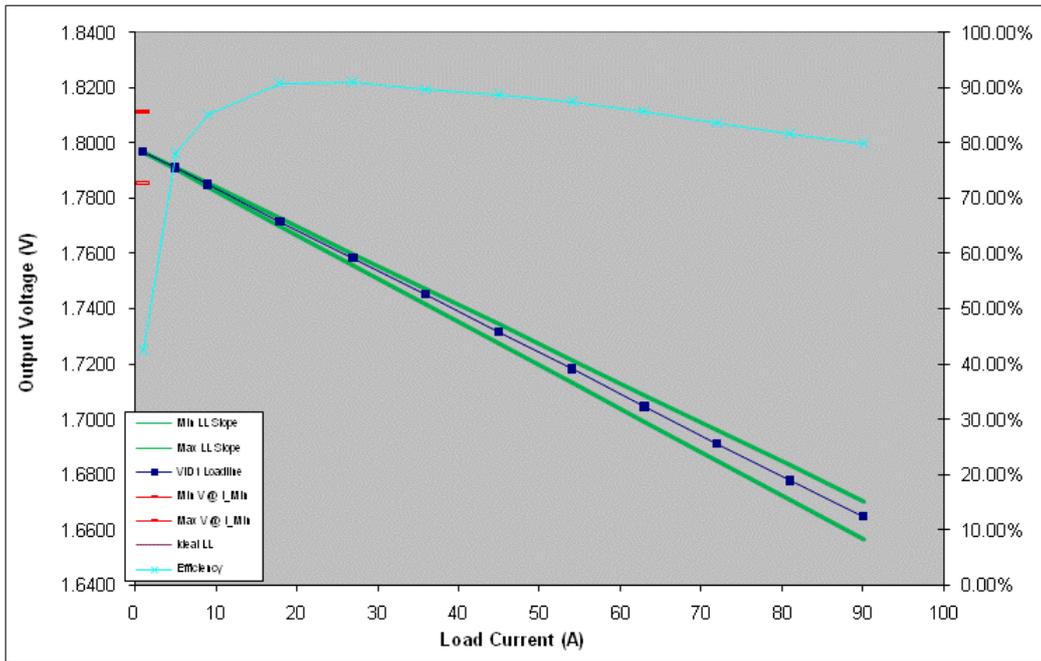


Figure 6. Measured load-line and efficiency from RT8884B.

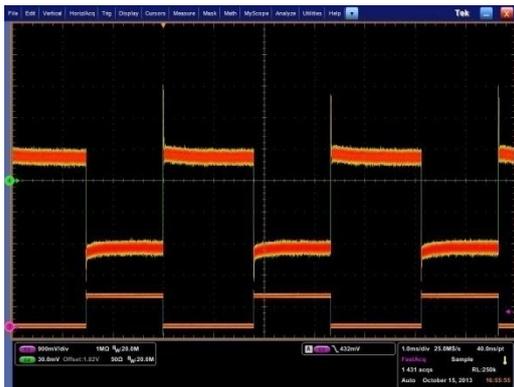

(a) Large step (1A-61A) ACLK @300Hz



(b) Small step (50A-60A) ACLK @300Hz

Figure 7. Measured ACLK result from RT8884B.

3.2. Conclusion

The design of the system components usually needs to compromise between lots of restrictions to gain the most benefit on the efficiency and performance. Besides, the particular layout skills are used to minimize the effect of the parasitic component and avoid the high speed switching noise coupling. This application note shows the general design approach of G-NAVP™ control topology and the PCB layout rules. Following the rules mentioned above, users can use Richtek’s controller IC without any inconvenience.

4. Reference

- [1] Richtek, RT8884B datasheet.
- [2] Intel document, “Shark Bay Ultrabook™ Platform Power Delivery”
- [3] Intel document, “Shark Bay Mobile Platform Power Delivery”
- [4] Intel document, “Shark Bay Desktop and Denlow-WS Platform”

Richtek Technology Corporation

14F, No. 8, Tai Yuen 1st Street, Chupei City
Hsinchu, Taiwan, R.O.C.
Tel: 886-3-5526789

Richtek products are sold by description only. Richtek reserves the right to change the circuitry and/or specifications without notice at any time. Customers should obtain the latest relevant information and data sheets before placing orders and should verify that such information is current and complete. Richtek cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Richtek product. Information furnished by Richtek is believed to be accurate and reliable. However, no responsibility is assumed by Richtek or its subsidiaries for its use; nor for any infringements of patents or other rights of third parties which may result from its use. No license is granted by implication or otherwise under any patent or patent rights of Richtek or its subsidiaries.